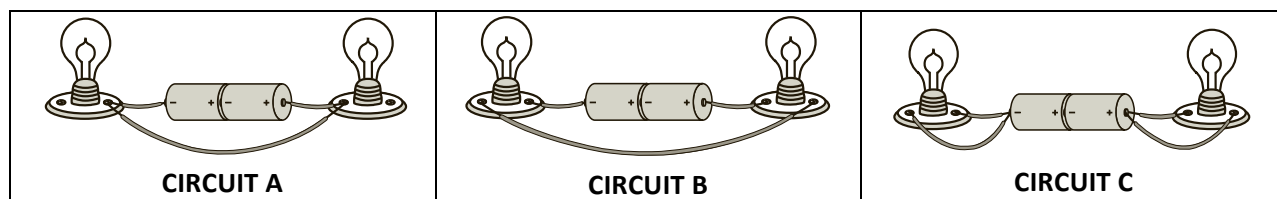


Common Writing Assignment: Science

Which circuit will light two bulbs?

Amanda thinks she could build a circuit that will light two bulbs. She is going to test these three circuit designs:



Using what you have learned from your work with electrical circuits, explain which circuit will light the bulbs. Use evidence to support your claim and explain your reasoning. Be sure to include why the other two circuits will not light.

Don't Forget to...

Plan your writing using an outline, web or graphic organizer. As you write each draft of your assignment, it's important to use what you know as a writer to communicate your ideas effectively.

- ✓ Provide a clear claim that answers the question.
- ✓ Include evidence -- using data from class activities, experiments and other resources.
- ✓ Include reasoning to show how your evidence supports your claim.
- ✓ Use vocabulary that you have learned in science class.
- ✓ Check for grammar, punctuation, and spelling errors.